

## Topic 15 - DC Circuits

### 1 Series and parallel arrangement

#### 1.1 Equivalent resistance

It is possible to replace a **combination of resistors** in any given circuit with a single resistor without altering the p.d. and the current across the terminals of the combination. The resistance of the single resistor is called the **equivalent resistance** of the combination

#### 1.2 Resistor in series

The current  $I$  through each resistor is the same

$$R = R_1 + R_2 + R_3 + \dots R_n$$

#### 1.3 Resistor in parallel

The p.d.  $V$  through each resistor is the same

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \frac{1}{R_n}$$

#### 1.4 Combination of E.M.F. cells in series

$$E_{total} = E_1 + E_2$$

#### 1.5 Combination of E.M.F. cells in parallel

For two cells with emf  $E_1$

$$E_{total} = E_1$$

## 2 Potential divider

For a circuit with emf  $V_s$  and 2 external loads  $R_1$  and  $R_2$  and current  $I$   
The current is given by

$$I = \frac{V_s}{R_1 + R_2}$$


The potential difference across  $R_1$  is thus

$$V_o = IR_1 = \left( \frac{R_1}{R_1 + R_2} \right) V_s$$


## 3 Potentiometer
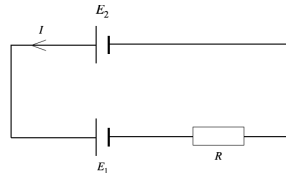
### 3.1 Working principles of a potentiometer

For the circuit below,  $I = 0$  when  $E_1 = E_2$



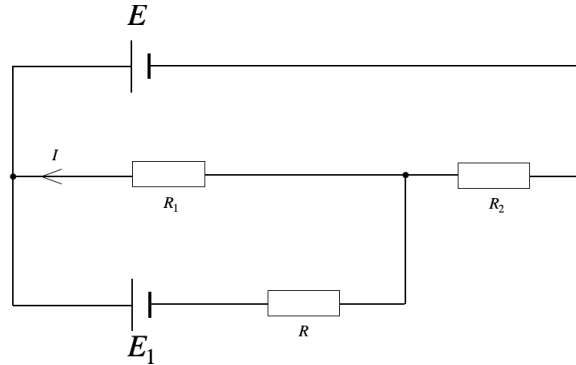
Replacing  $E_2$  with a potential divider circuit,



By varying  $R_1$  and  $R_2$ , no current flows through  $E_1$  when the *p.d.* across  $R_1$  is equal to  $E_1$
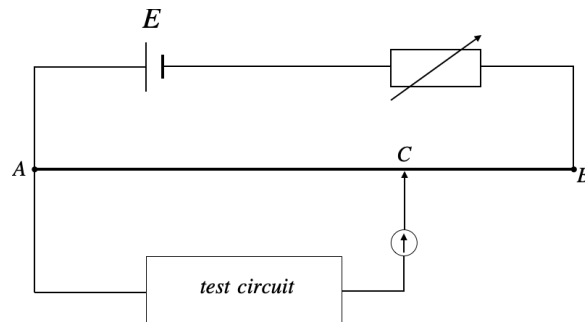
### 3.2 Null point, balance point and balance length

By replacing  $R_1$  and  $R_2$  with a resistance wire  $AB$  and a sliding contact at point  $C$ , the galvanometer shows no reflection at **null point** or **balance point**.  $AC$  is the **balance length**.



Assuming

- Wire  $AB$  has uniform cross sectional area
- Potential difference across wire remains constant with time

For a **uniform wire** of length  $L$ ,

$$R = \frac{\rho L}{A}$$

$$R \propto L$$

The potential difference across  $AC$  is


$$V_{AC} = \frac{R_{AC}}{R_{AB}} \times V_{AB}$$

$$V_{AC} = \frac{L_{AC}}{L_{AB}} \times V_{AB}$$

### 3.3 Voltmeter vs potentiometer

- for potentiometer, no errors are introduced by internal resistance of the cells (since no current flows through the cells at balance length)
- real voltmeter has **finite resistance**, and hence draws a current from the cell, and lowers the terminal p.d. of the cell when connected
- for potentiometer, since **no current flows at balance point**, the potentiometer can be considered to be a voltmeter with **infinite resistance**
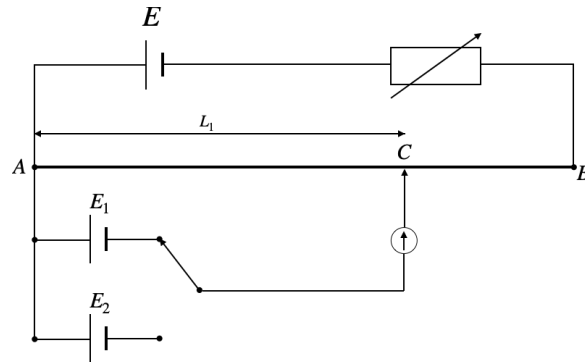
### 3.4 Application 1 - Comparison of e.m.fs



Since at balance length,

$$E_i = \frac{R_{AC}}{R_{AB}} \times V_{AB}$$

Since  $V_{AB}$  and  $R_{AB}$  constant,


$$E_i = kL_i$$

hence

$$\frac{E_1}{E_2} = \frac{kL_1}{kL_2} = \frac{L_1}{L_2}$$

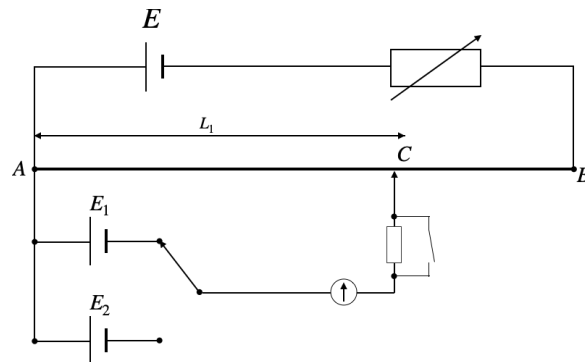
#### NOTE - shorting key as a protection for galvanometer

To ensure precision of potentiometer, the galvanometer used is very sensitive. The galvanometer should be protected from **high currents** that flows through in **off-balance** situations, by using a large resistance in series.



- Before approximate null point is reached, the shorting key is **left open**, to protect the galvanometer from large currents
- nearing the null point, the key is **closed**, to allow for full current to flow through, so that an accurate balance point can be found
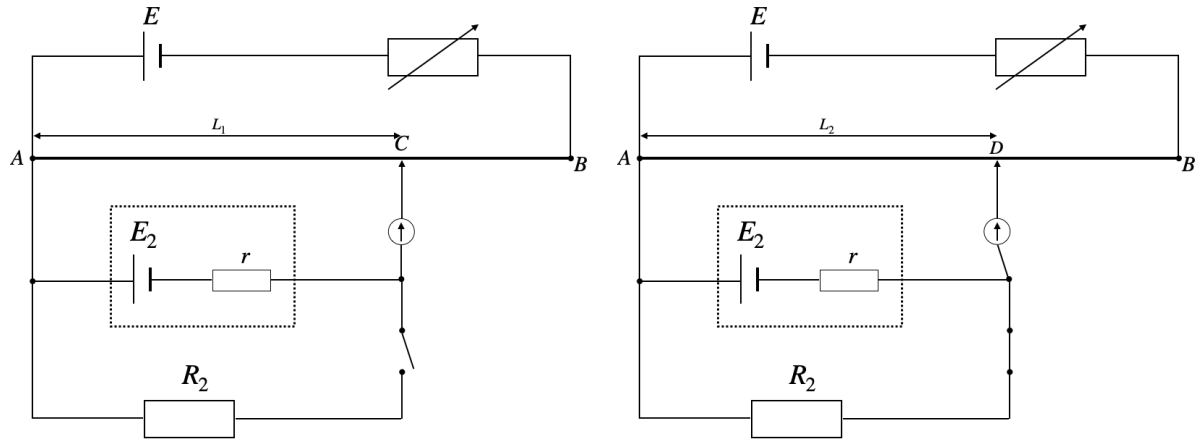
### 3.5 Application 2 - Measuring e.m.f. and internal resistance of a cell



- when **switch is open**,  $E_2$  can be found with  $L_1$

$$E_2 = \frac{L_1}{L_{AB}} \times V_{AB}$$

- when switch is closed, there is a current flowing through  $E_2$

$$\text{terminal p.d. across } E_2 = \text{terminal p.d. across } R_2 = \frac{L_2}{L_{AB}} \times V_{AB}$$


- the current flowing through  $R_2$  is

$$I = \frac{V}{R_2} = \frac{L_2}{L_{AB}} \times V_{AB} \times \frac{1}{R_2}$$

- the internal resistance can be found by

$$V = E_2 - Ir$$
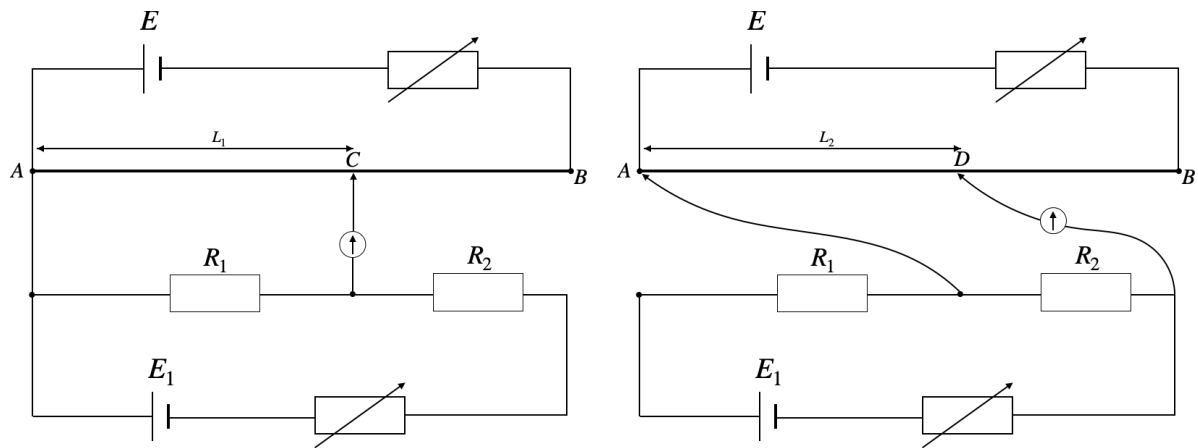
### 3.6 Application 3 - Comparison of resistance of two resistors



p.d. across  $R_1$  is,

$$V_1 = \frac{L_1}{L_{AB}} \times V_{AB}$$

p.d. across  $R_2$  is

$$V_2 = \frac{L_2}{L_{AB}} \times V_{AB}$$

hence in the test circuit

$$IR_1 = \frac{L_1}{L_{AB}} \times V_{AB}$$

$$IR_R = \frac{L_R}{L_{AB}} \times V_{AB}$$

since current  $I$  is the same

$$\frac{R_1}{R_2} = \frac{L_1}{L_2}$$